

# DEVICES AND COMMUNICATION BUSES FOR DEVICES NETWORK—

## Lesson-8: Parallel Port Interfacing with a Stepper Motor

# Port Interfacing — Parallel port outputs O0 to O7

- Four outputs may be used as driver to four coils of a stepper motor

# Stepper-motor rotation

- One step angle when its four coils are given the currents in a specific sequence and that sequence is altered.
- Assume that currents at an instance equal  $+i, 0, 0, 0$  in four coils  $X, X', Y, Y'$ . The motor rotates by one step when the currents change to  $0, +i, 0, 0$ .

# Forward motion Sequences at the intervals of $T$

- Sequences at the intervals of  $T$  changed as follows: 1000, 0100, 0010, 0001, 1000, 0100, .... [The bits in the nibble (set of 4 bits) rotate by right shift.]
- Here 1 corresponds to  $+i$ .
- The motor rotation  $n$  step angles in interval =  $(n.T)$ .

# Reverse motion Sequences at the intervals of $T$

- Sequences changed to rotate the motor in reverse direction
- 0001, 00010, 0100, 1000, 0001, 0010, ....[The bits in the nibble (set of 4 bits) rotate by left shift.]

## Half Angle Change

- Coils are given the currents in the sequences of 1100, 0110, 0011, 1001, 1100, 0110, .... or 0011, 0110, 1100, 1001, 0011, 0110, ....
- The motor rotates  $(n/2)$  steps in interval =  $(n.T/2)$ . T is the period of clock pulses, which drive the motor by change of coil currents to next sequence.

# Port Interfacing


- 4 coils connect to parallel-port 4 outputs

## Stepper motor driver— a processing element

- **Driver** is given two outputs from the port— clock pulses and rotating direction bit  $r$ . For example, if  $r = 1$ , the motor rotates clockwise and 0 then anti-clockwise. The motor rotates as long as clock pulses are given at the output pin.


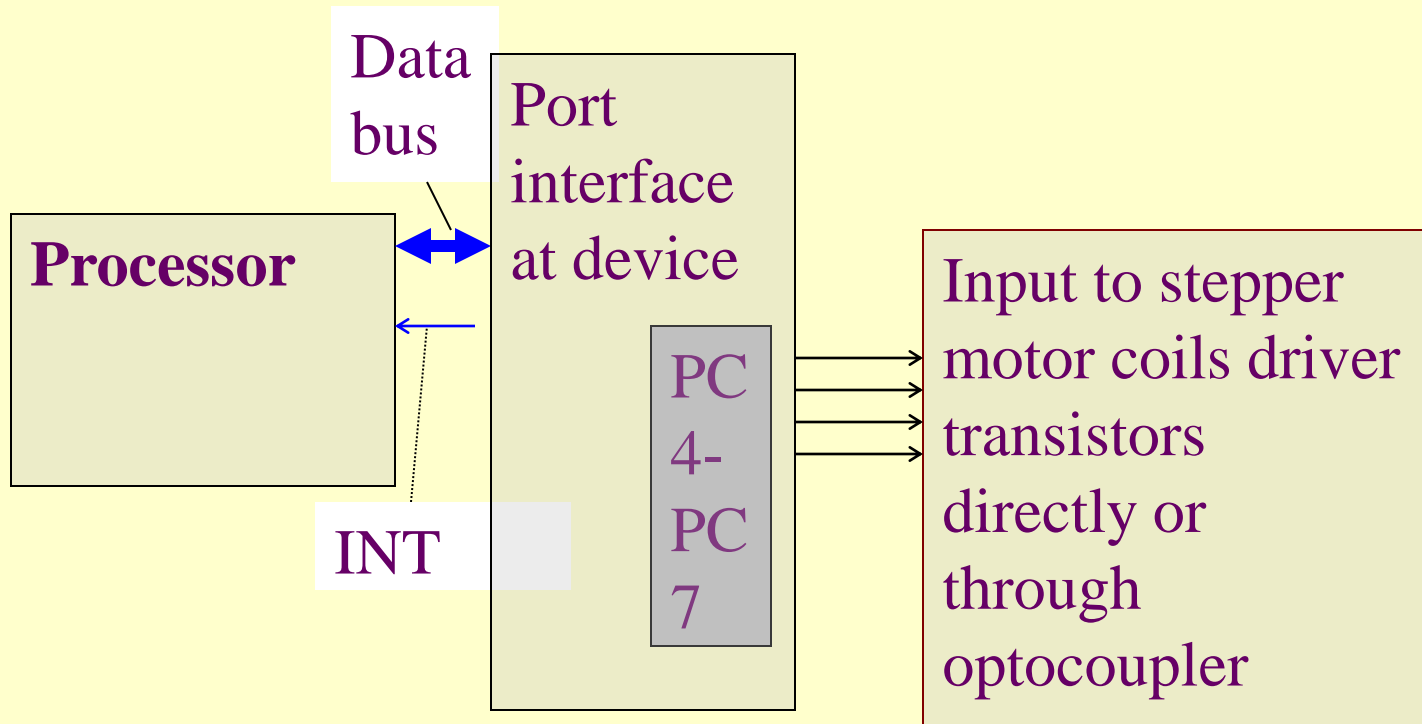
# Four-bit parallel output port C connected to a stepper motor



# Summary

We learnt

- Stepper motor four coils
- Sequences of current inputs to the coils

## We learnt

- 1000, 0100, 0010, 0001, 1000, 0100, ....

Full step forward

- 0001, 00010, 0100, 1000, 0001, 0010, ....

Full step reverse

- 1100, 0110, 0011, 1001, 1100, 0110, ....

Half step forward

- 0011, 0110, 1100, 1001, 0011, 0110, ....

Half step reverse

End of Lesson 8 of Chapter 5  
on  
Parallel Port Interfacing  
with a Stepper Motor