

Chapter 7

System Design: Peripheral ICs and Interfacing

Lesson 5

ADC - Analog to Digital Converter

Analog to Digital Conversion (ADC)

- Need of Analog signal to be converted into bits in many applications
- Need a reference input (V_{ref+}) = The maximum input when after conversion output bits= all 1s)
- Need V_{ref-} = The minimum input when after conversion output bits= all 0s)
- Generates Digital output bits proportional to the ADC analog input

ADC output after conversion of analog signal

- n-bit ADC (output) = binary number for

$$\frac{\text{Analog input} * \{(2^n) - 1\}}{(V_{\text{ref}+} - V_{\text{ref}-})}$$

8-bit ADC example

- Assume that 8-bit ADC $V_{ref+} = 1.275 \text{ V}$ and $V_{ref-} = 0 \text{ V}$.
- Output bits = all 0s = 00000000 (=0d) when input = 0V,
- Output bits = 10000000 (= 128d) when input = 0.64V and
- Output bits = 11111111 (= 255d) when input = 1.275V

Example of ADC in a Microcontroller

- 80535 ADC with programmable voltage reference
- 80552 10-bit ADC with 8-ch AMUX (Analog multiplexer- same ADC with multiple analog input channels)

Example of ADC in a Microcontroller

- ADC04 one channel ADC with voltage reference = $1/2$ of maximum permitted analog input
- ADC0808 eight channels ADC with voltage reference + and -inputs
- ADC0816 sixteen channels

Considerations when using an ADC

- Number of bits
- Reference Input single or dual
- Reference programmable or non programmable
- Multi or single channel
- Conversion accuracy
- Sampling rate
- Data throughput rate
- CMOS or Bipolar based

Condition when using an ADC

- Separate analog ground
- Location nearest possible to a signal transducer

ADC0804

- 8 bit ADC
- Interfaces with microcontroller ports or processor data and control bus signals
D0-D7, RD and WR and INTR
- Requires $V_{ref}/2$ input
- Converted output = $1000\ 000_b$ output when analog input = $V_{ref}/2$
- WR input results in start of conversion (SOC)


ADC0804

- SOC_input— very short duration pulse (ns) using a NOT-NAND combination
- RD input results in converted bits at output at D0-D7 bus
- EOC output for end of conversion to to facilitate Interrupt (INTR) driven IO to the processor

ADC0804

- Separate analog and digital grounds to isolate digital transitions noise by direct connection of ANALOG-GND to supply GND
- Clock frequency adjustable by external RC pair timing constant

ADC One Channel Vin+ in ADC0804

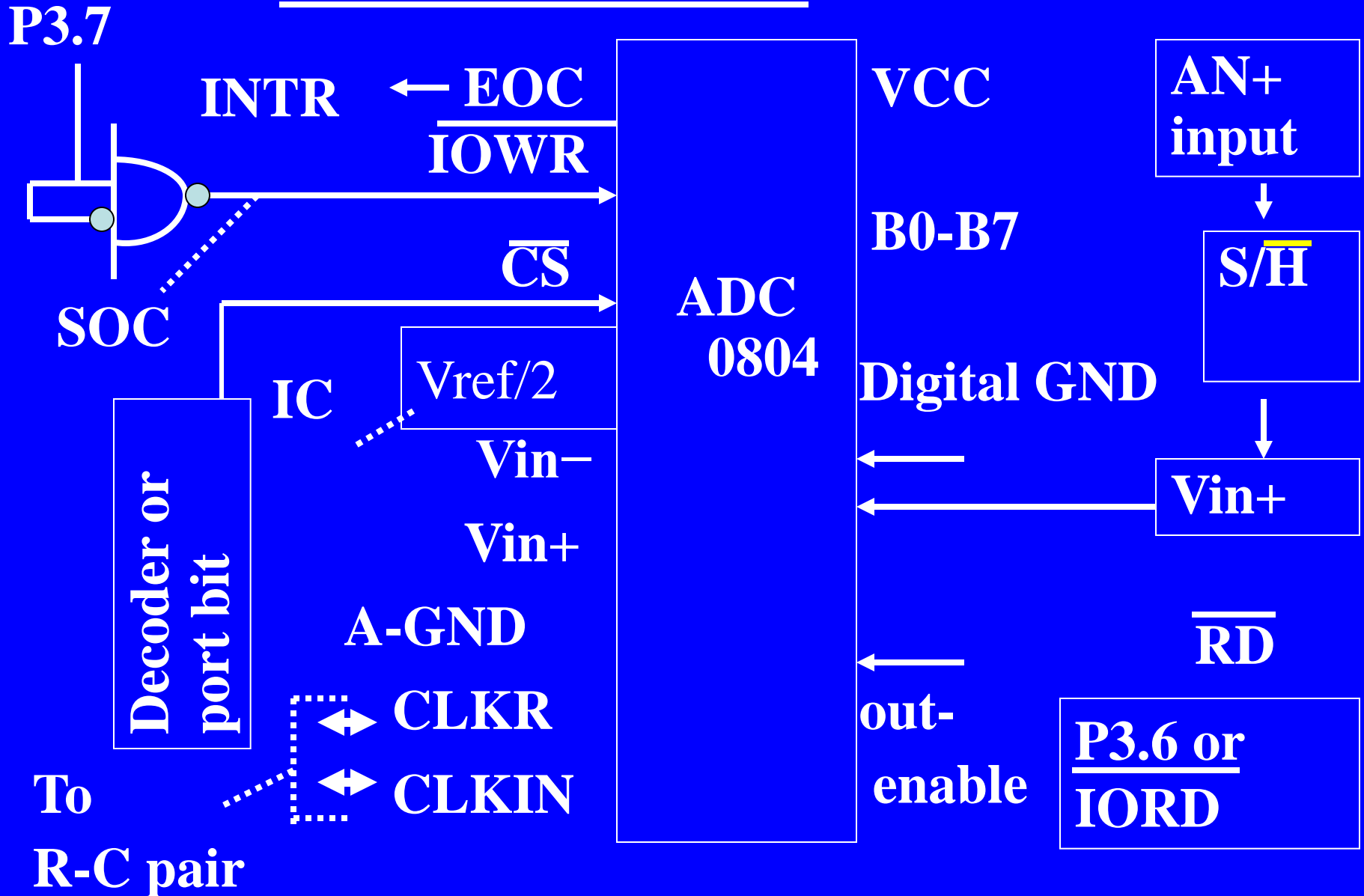

ADC0808

- 8 bit ADC
- Interfaces micro-controller ports or processor D0-D7, \overline{RD} , \overline{WR} , ALE (built in latch) for channel select through AD2-AD1-AD0 inputs
- Start of conversion (\overline{SOC}) using \overline{WR}


ADC0808

- SOC_input very short duration (ns) pulse using a NOT-NAND combination
- **output enable** for converted bits on D0-D7 using RD
- EOC output for end of conversion to facilitate interrupt (INTR) driven IO

ADC0808



- Separate analog and digital grounds to separate digital transitions noise by direct connection of A-GND to supply GND
- Clock frequency input

8 Channels ADC

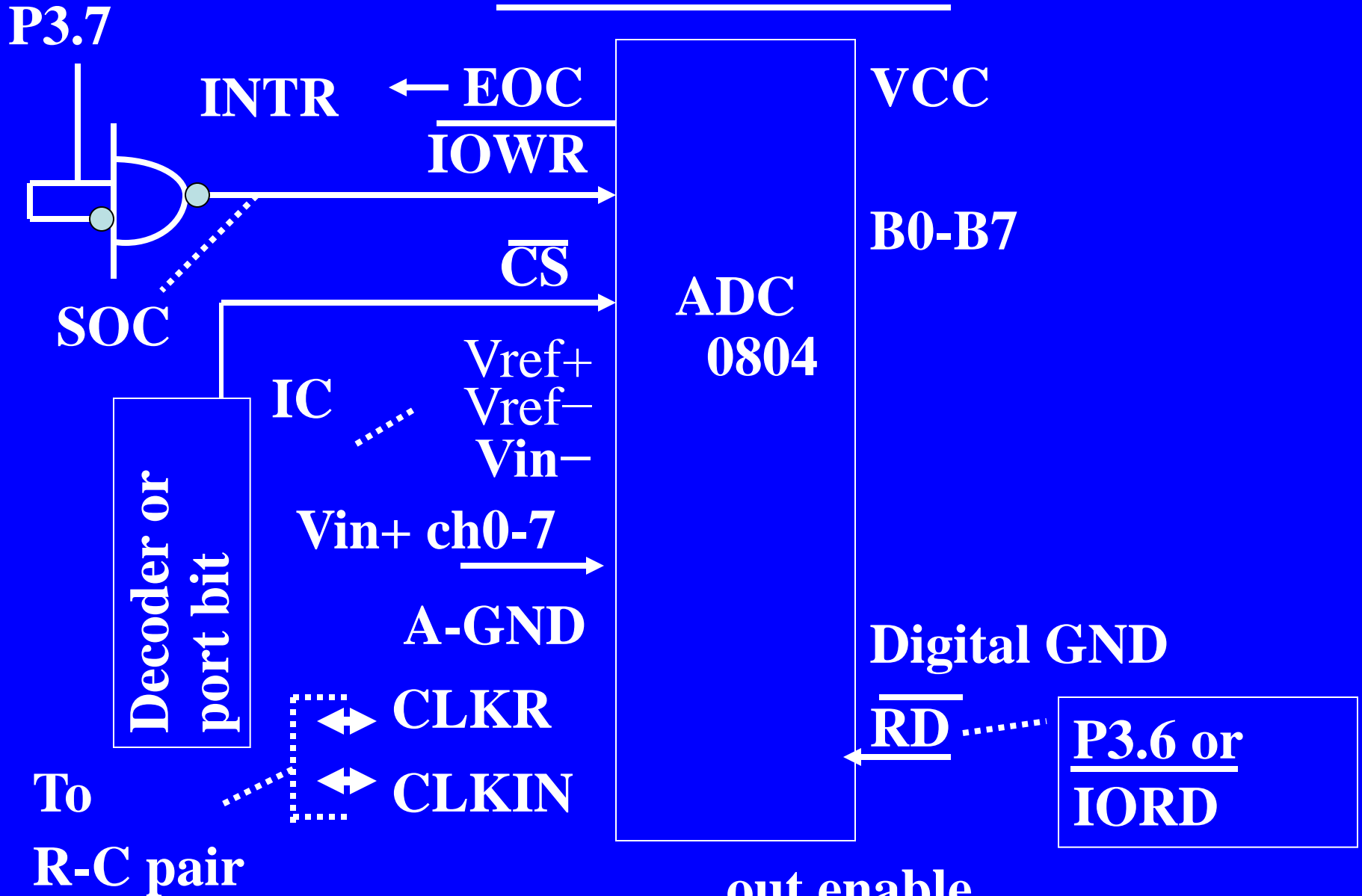

Interfacing ADC0808

B0-B7 connects to data AD0-AD7

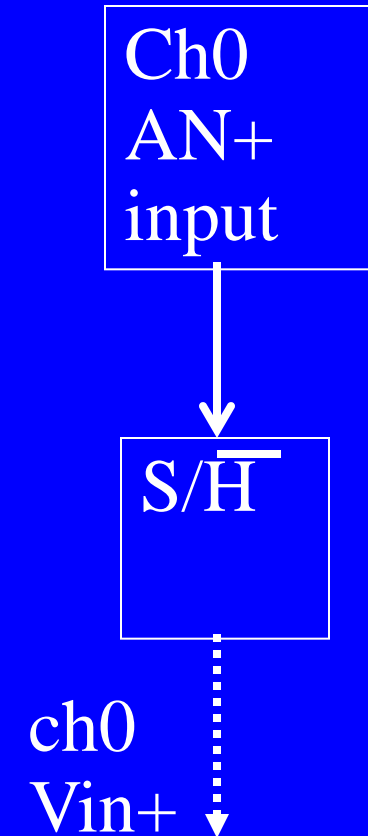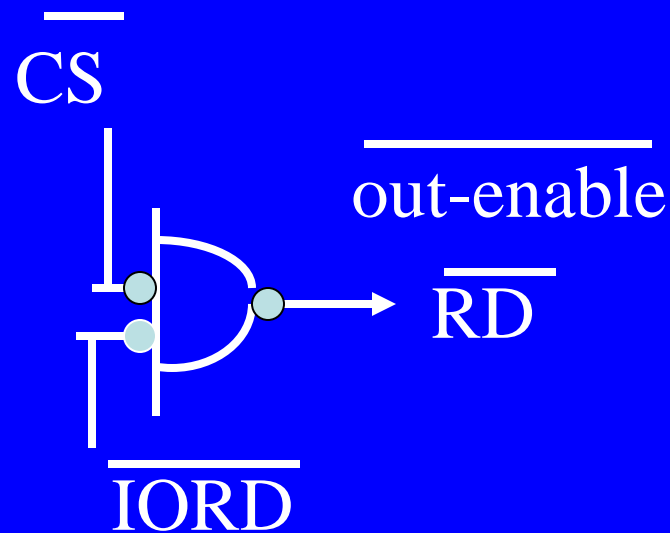

ADC0816

- 8 bit ADC
- Interfaces micro-controller ports or processor data buses (D0-D7), RD, WR, ALE for channel select through AD3-AD2-AD1-AD0 bus inputs (also separate A3-A0),
- WR input for start of conversion (SOC)

ADC0816

- Separate output enable input for expanding the number of channels
- Analog multiplexer in-built gives the analog output for the filter and S/\overline{H} inputs and then hold outputs to get analog inputs for conversion (External S/\overline{H} and filter not needed for channels)


ADC0816

- SOC input can be very short pulse (ns) using a NOT-NAND combination
- RD input for converted bits on D0-D7
- EOC output for end of conversion to facilitate **interrupt** (INTR) driven IOs

ADC0816

- Separate analog and digital grounds to separate digital transitions noise by direct connection of A-GND to supply GND
- Clock frequency input

ADC 16- Channels

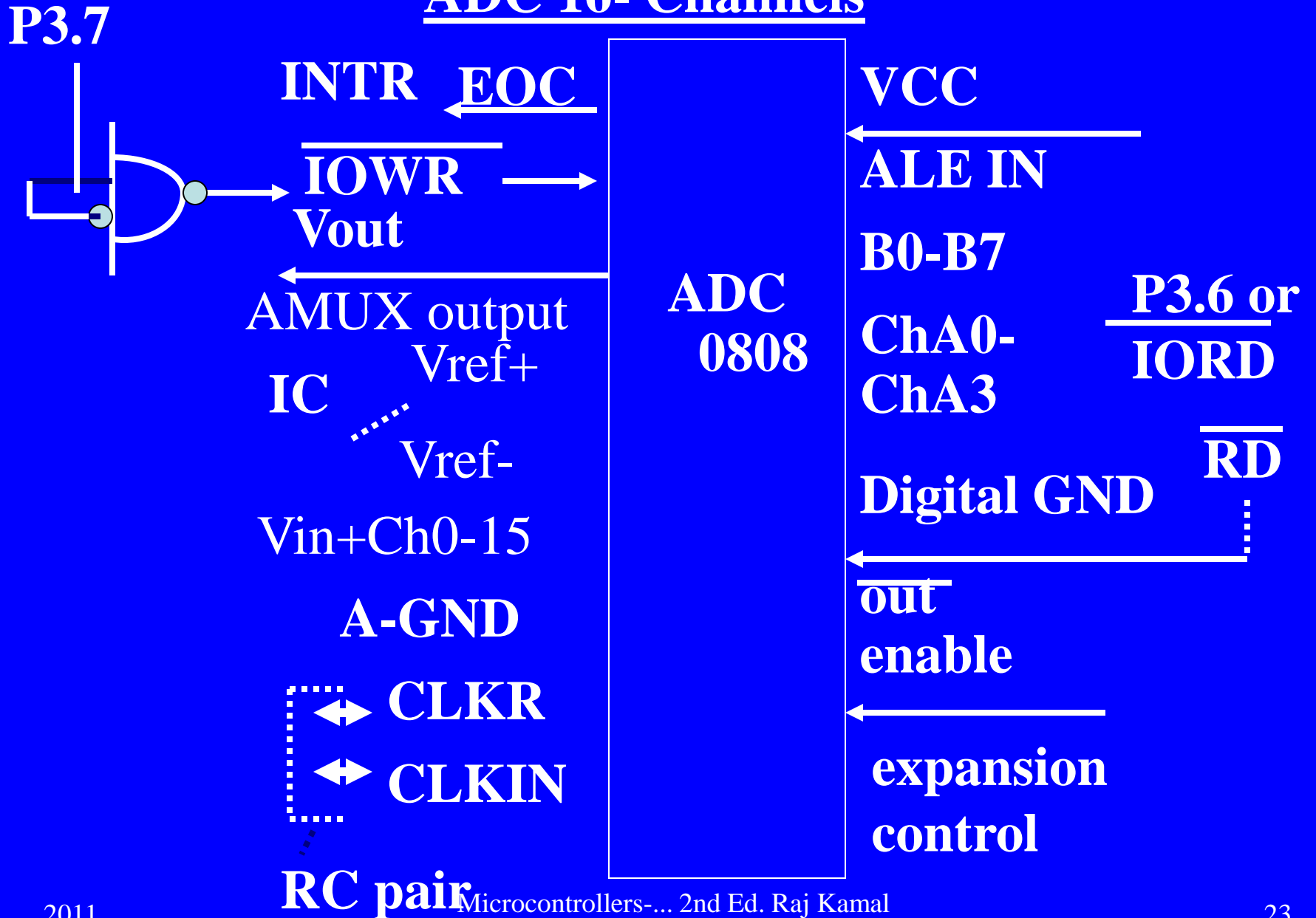

ChA0-ChA3 connects to A0-A3/AD0-AD3

ALE IN

B0-B7 connects to data D0-D7


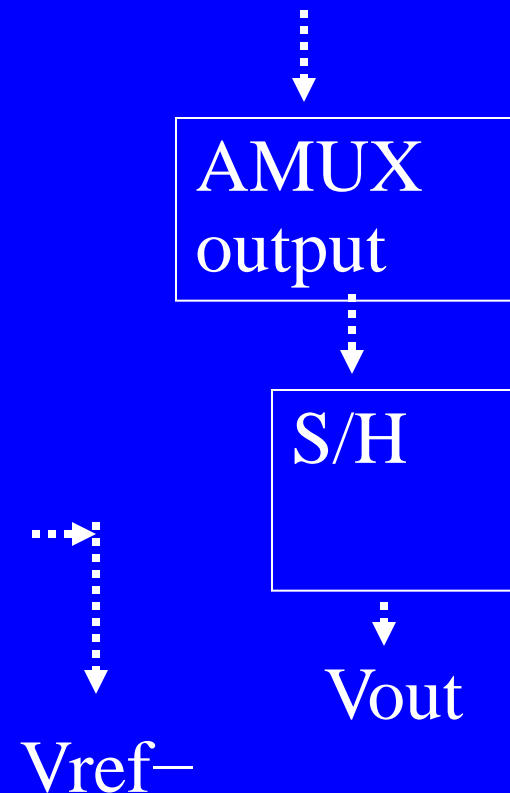
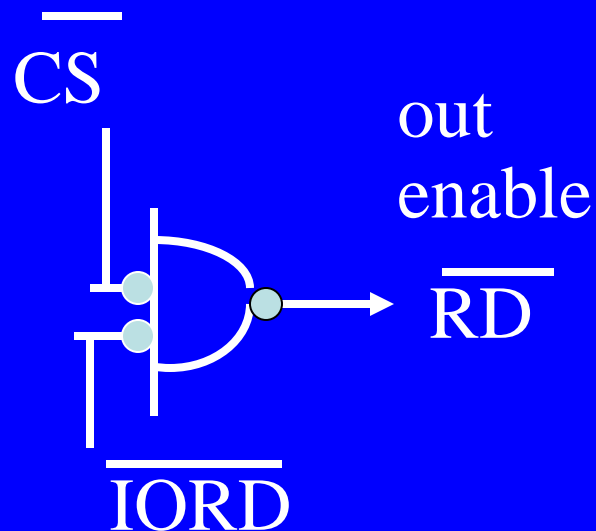


Table 7.19 - Functions of
subunits in circuit


Table 7.20 - Each Pin signals

A3-A2-A2-A1 Channel select bits

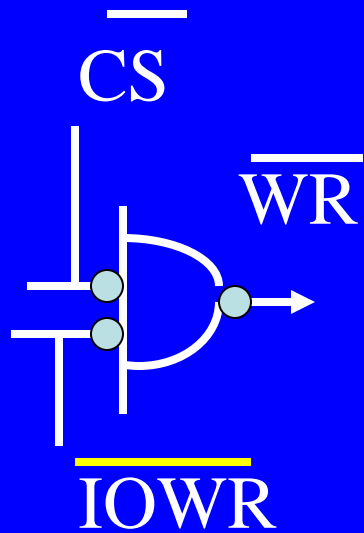


Table 7.21 - Sixteen Addresses in Exemplary circuit for ADC 08016, when interfacing using $A_n-A7 = 0$, $A6 = 1$ $A5 = 0$ $A4 = 0$

ADC0804 with 8051

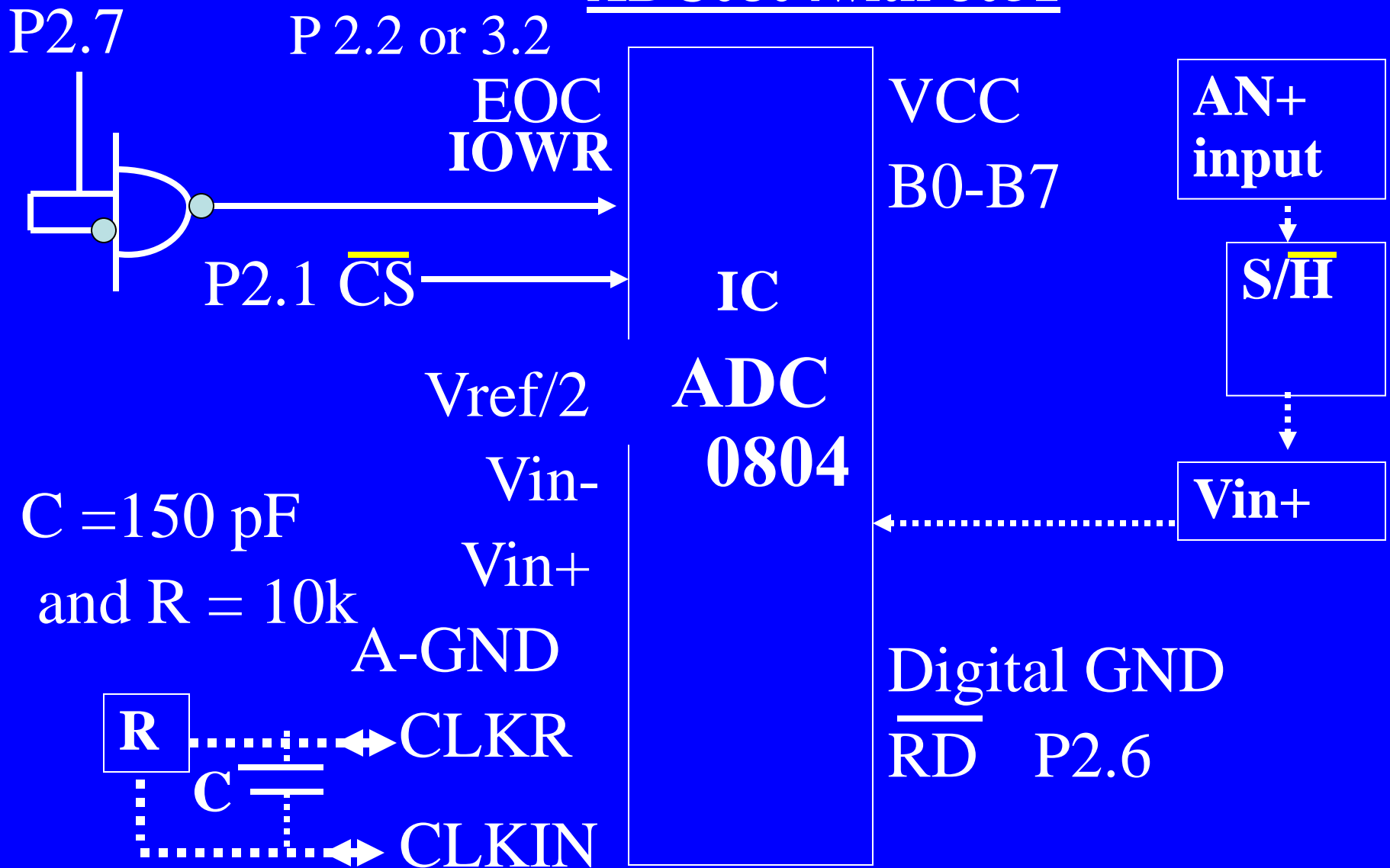

1. Initial condition $P2.6 = 1, P2.7 = 1, P3.2 = 1$
2. Select ADC write $P2.1 = 0$
3. Pulse Start ADC write $P2.7 = 1$, then $P2.7 = 0$
4. Wait till INT0 interrupt or till $P2.2$
5. Reset $P2.6$ and Read $P1$

Interface with 68HC11

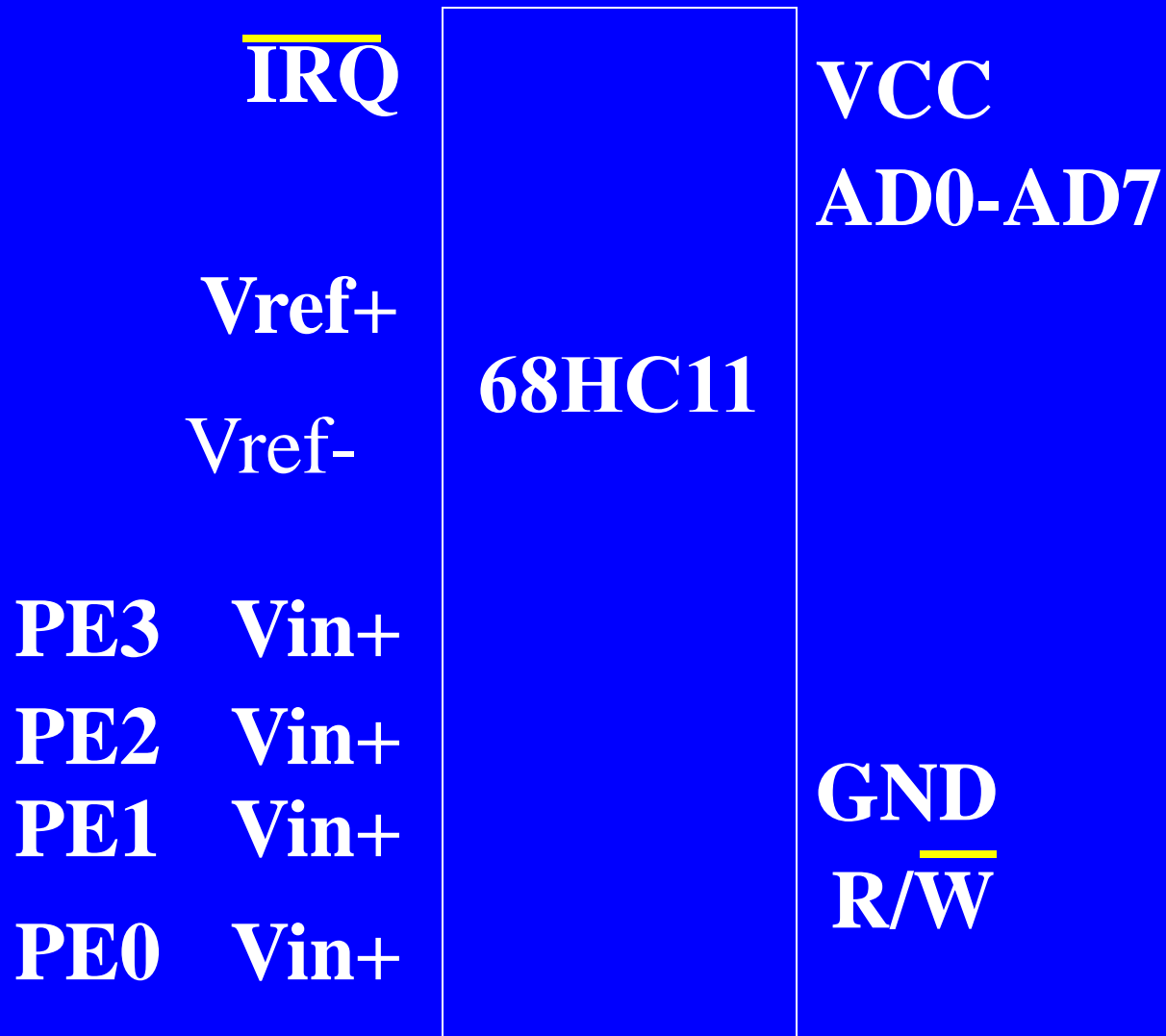

Summary

We learnt

- ADC Bits at output
- ADC 0804,0808, 0816
- Internal AMUX and channel address latch
- Multi channel ADC
- ADC Interfacing to ports