


Chapter 8

Digital and Analog Interfacing Methods


Lesson 10

Interfaces for the High Power Devices


d.c. I/O Module

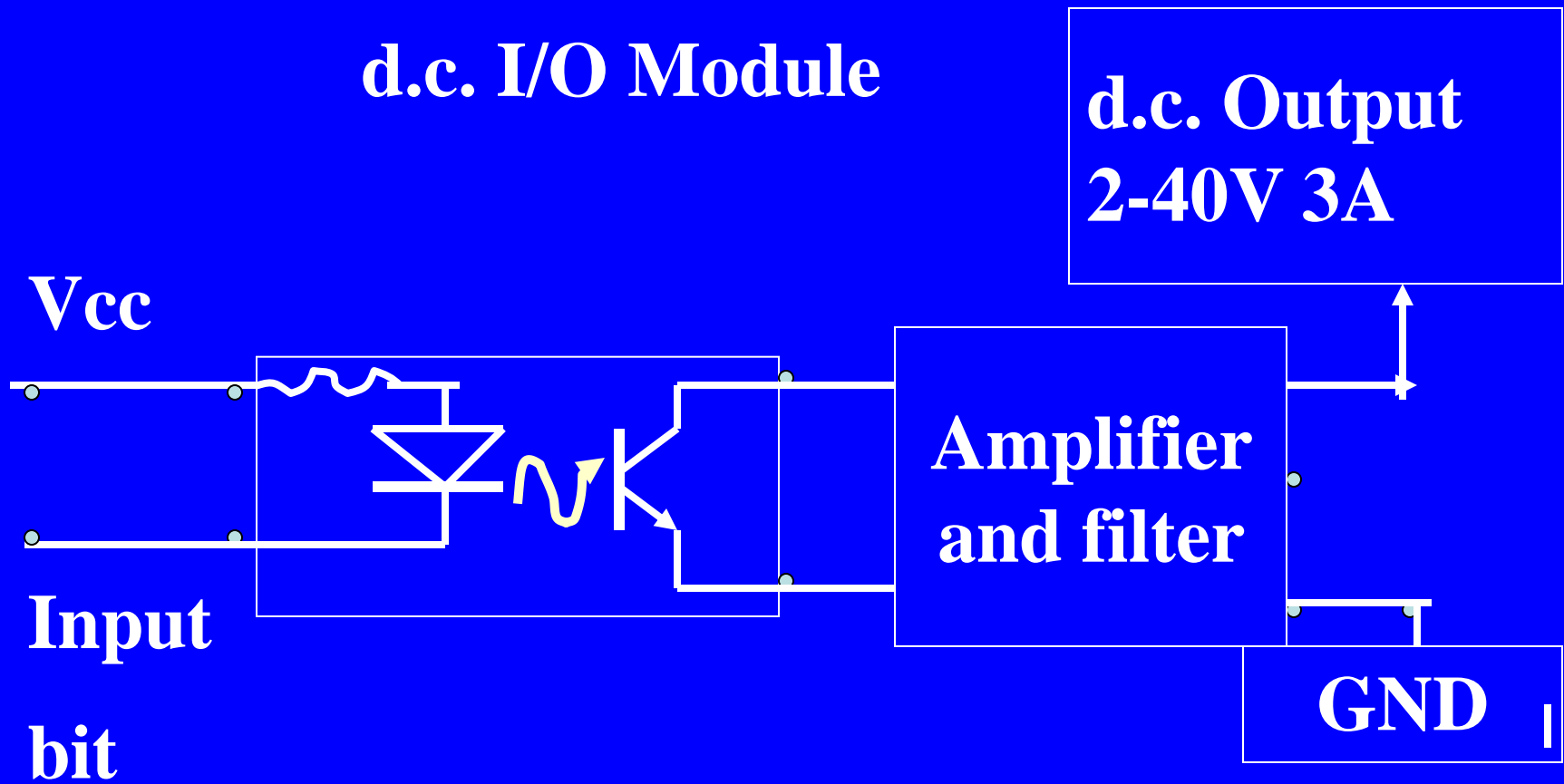

d.c. I/O Module

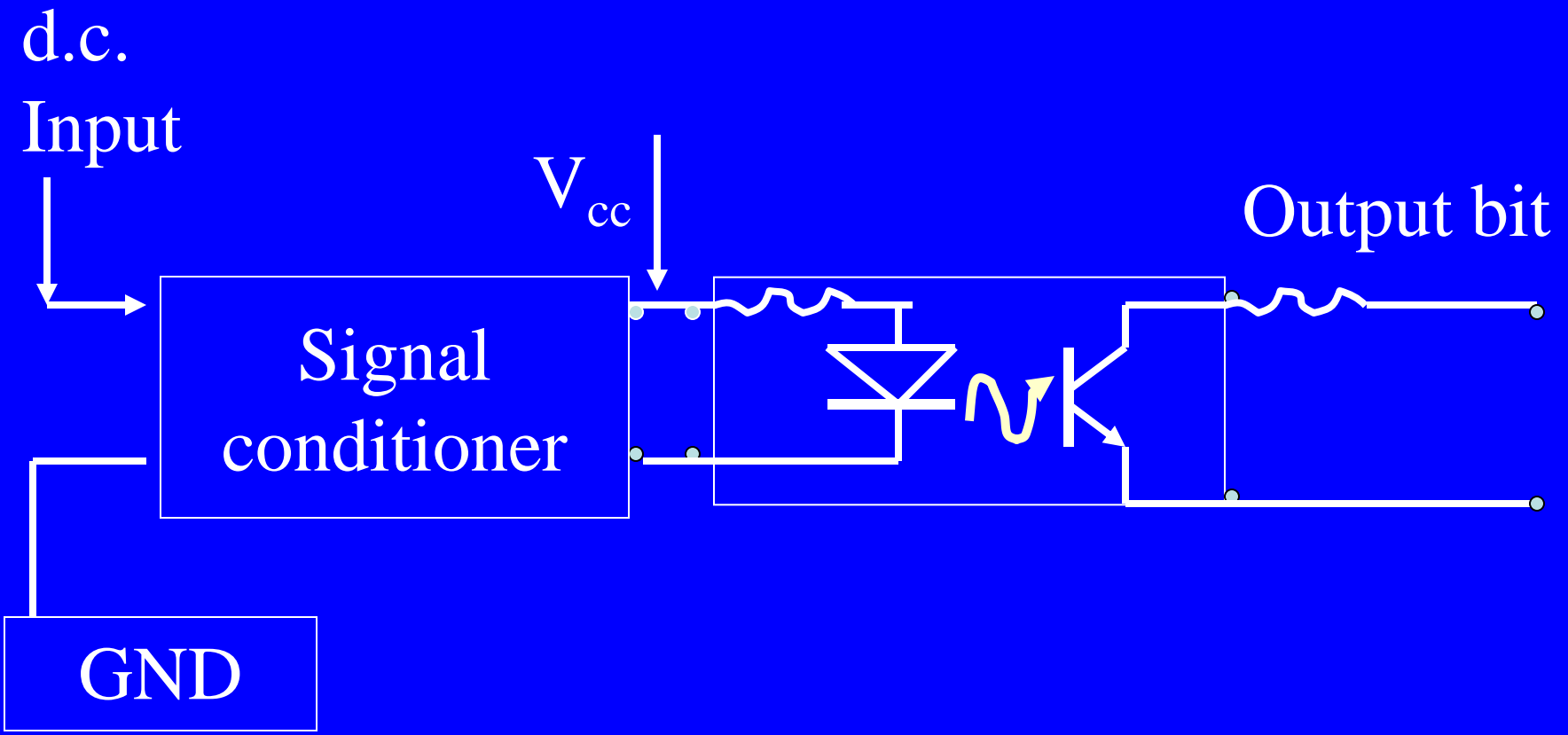


a.c. I/O Module

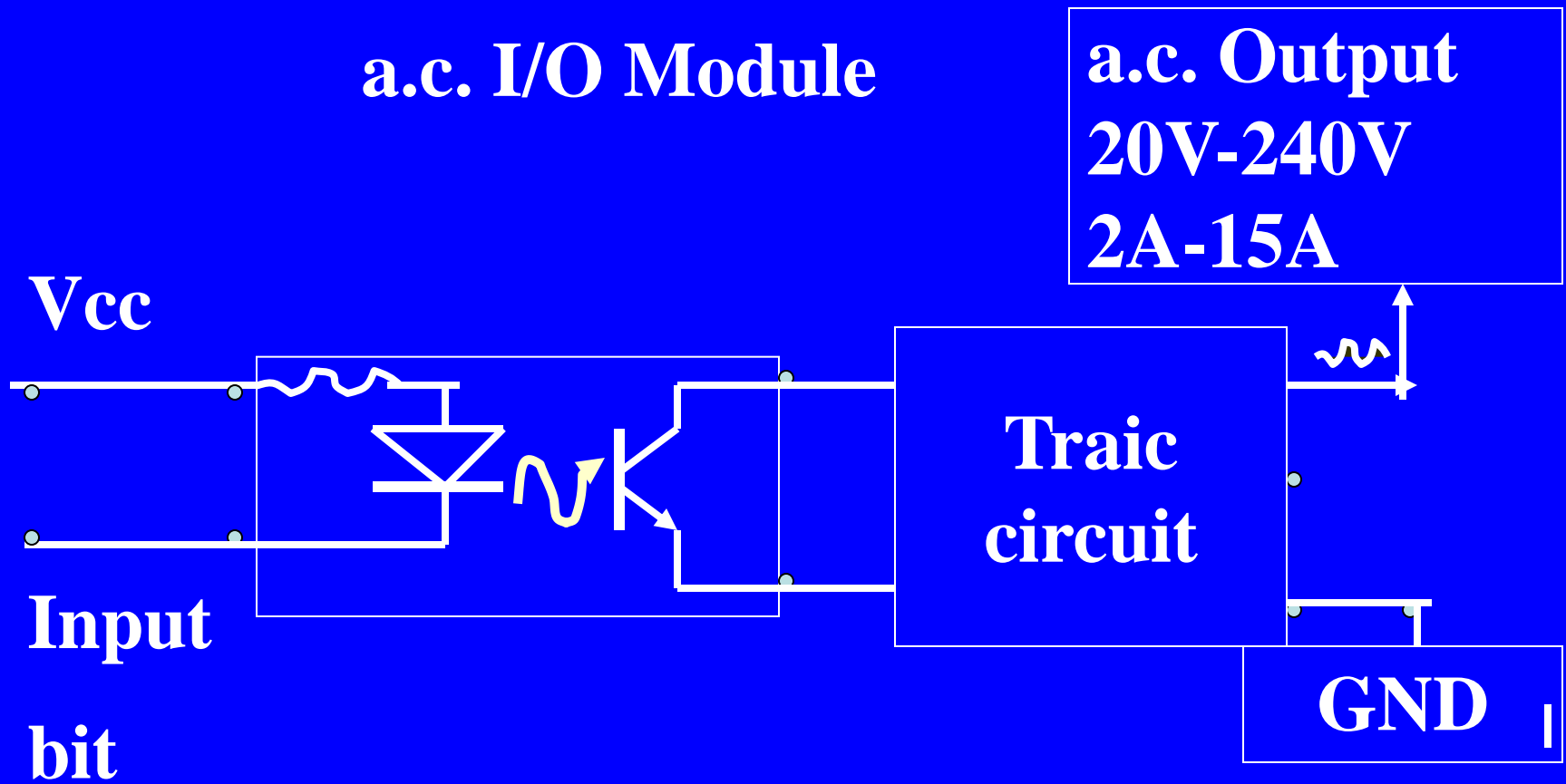

a.c. Input 20V-
240V/ 2A source

a.c. I/O Module

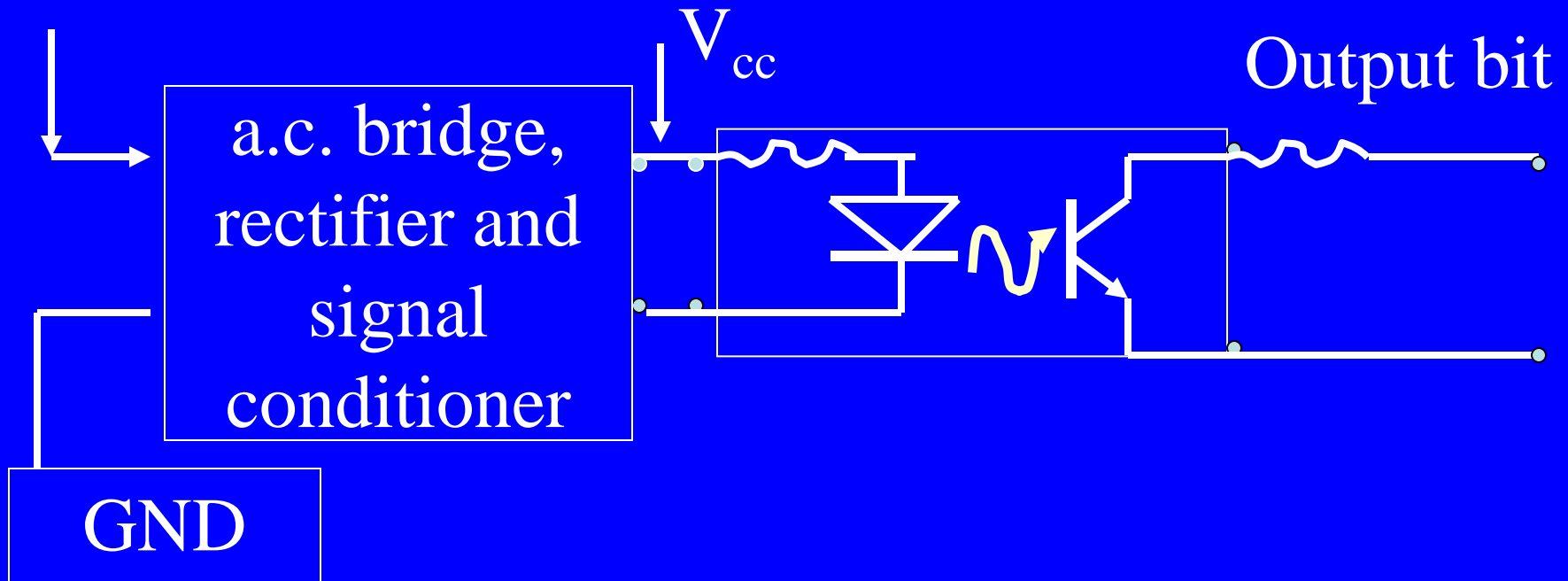

I/O Module inner parts

- Opto-isolator,
- Amplifier,
- Input stage Signal conditioning amplifier or input stage bridge
- Output stage transistor or triac circuit


I/O Module Optical Isolation - Protection and Isolation

- (1) Transient surges
- (2) Larger Signal inputs (For example, ~30V)
- (3) Mistakes like an input shorted to the power line (220V or 110V)


I/O Module Optical Isolation - Protection and Isolation

(4) Large Input Offsets, for example 440V


d.c. input Module

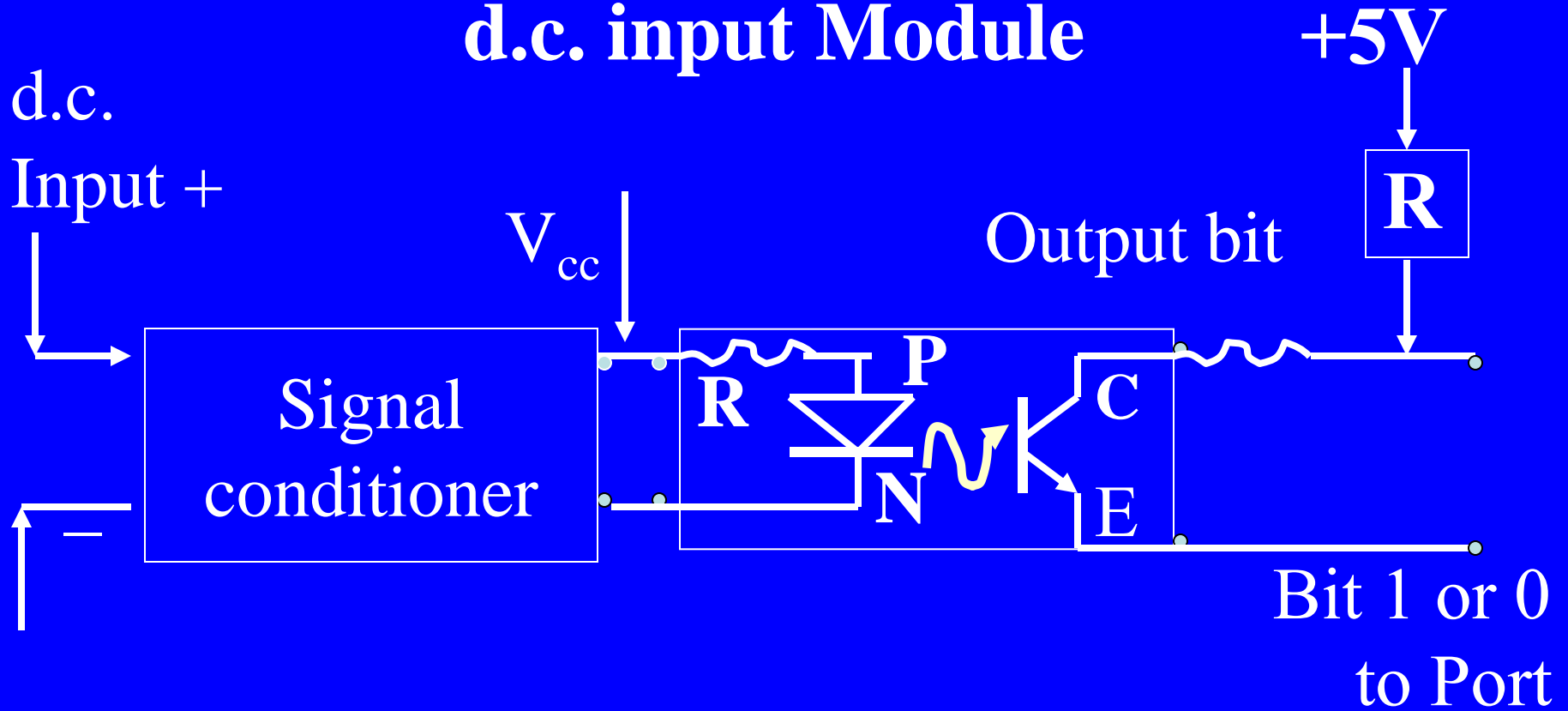


a.c. input Module

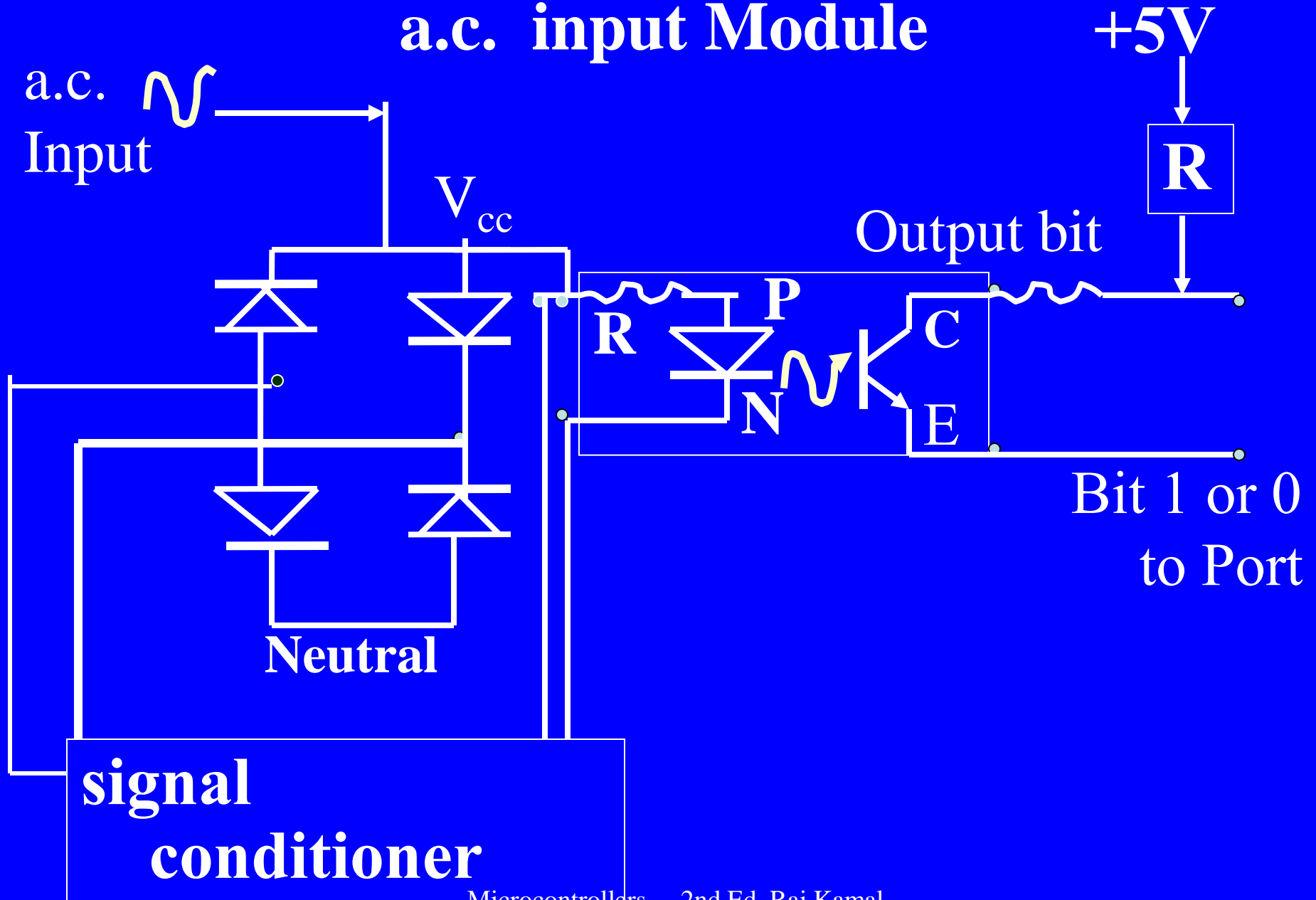

d.c. I/O Module

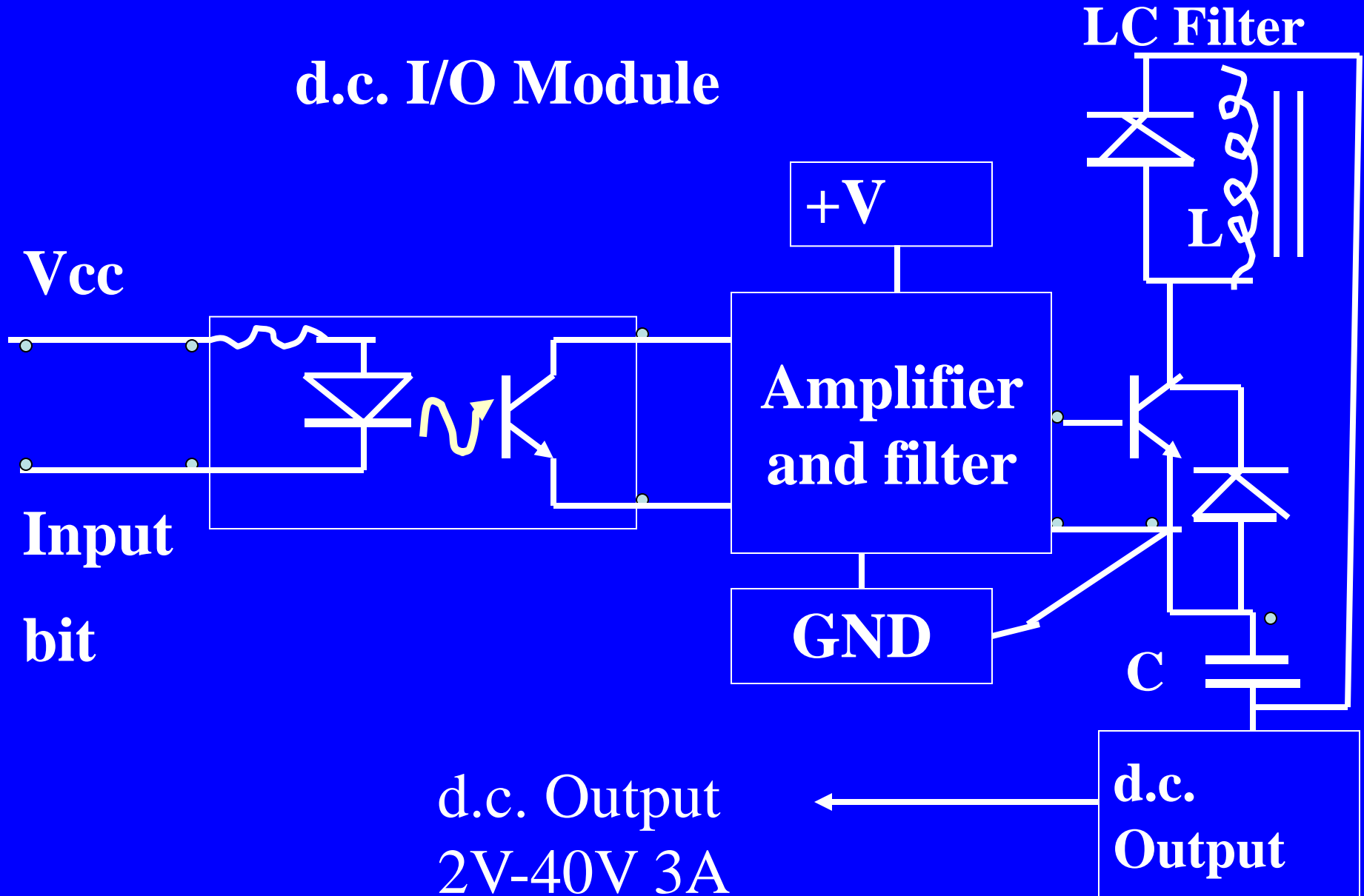


a.c. I/O Module

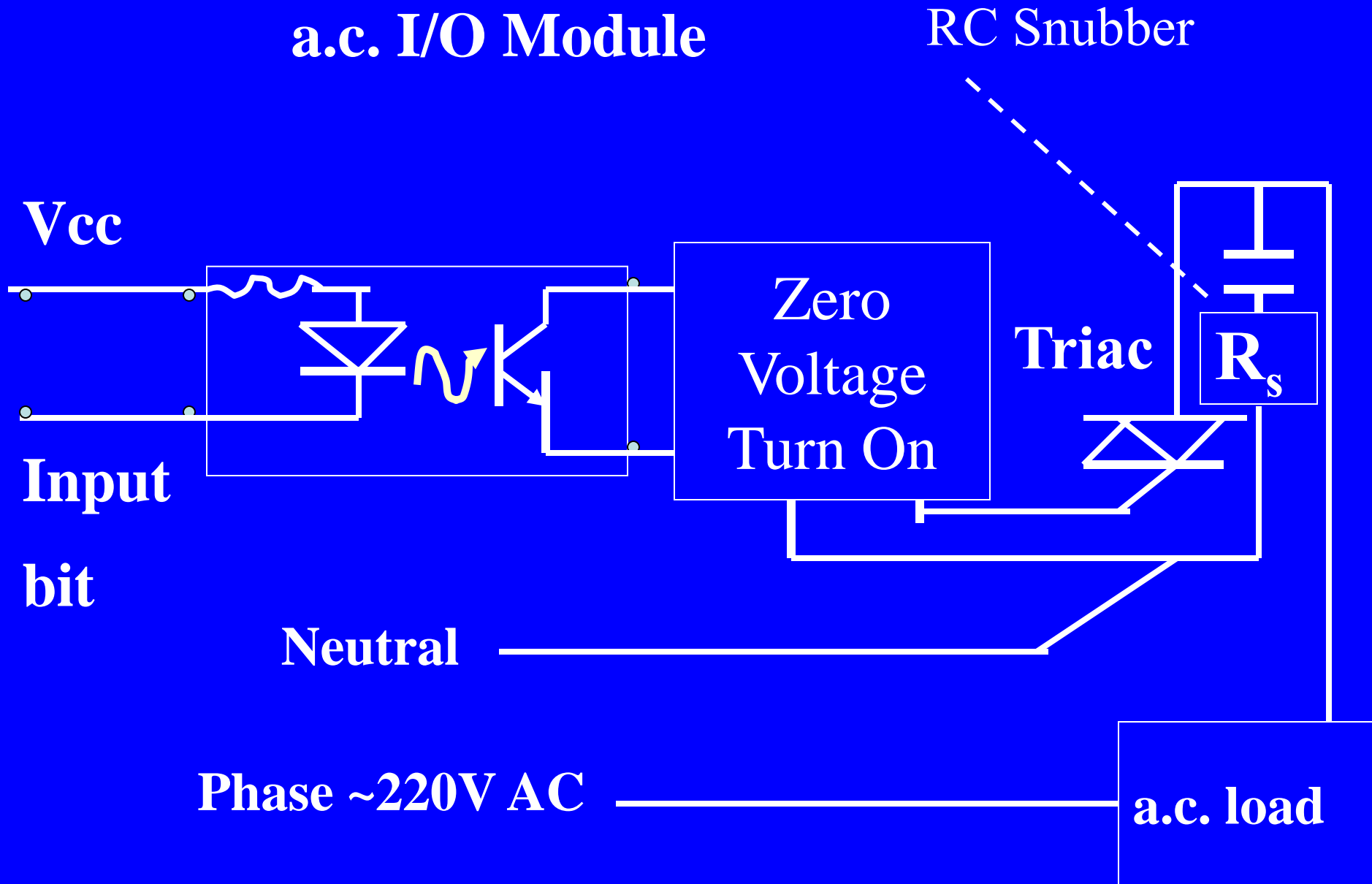


Exemplary circuits for the motor and heater


a.c. I/O Module

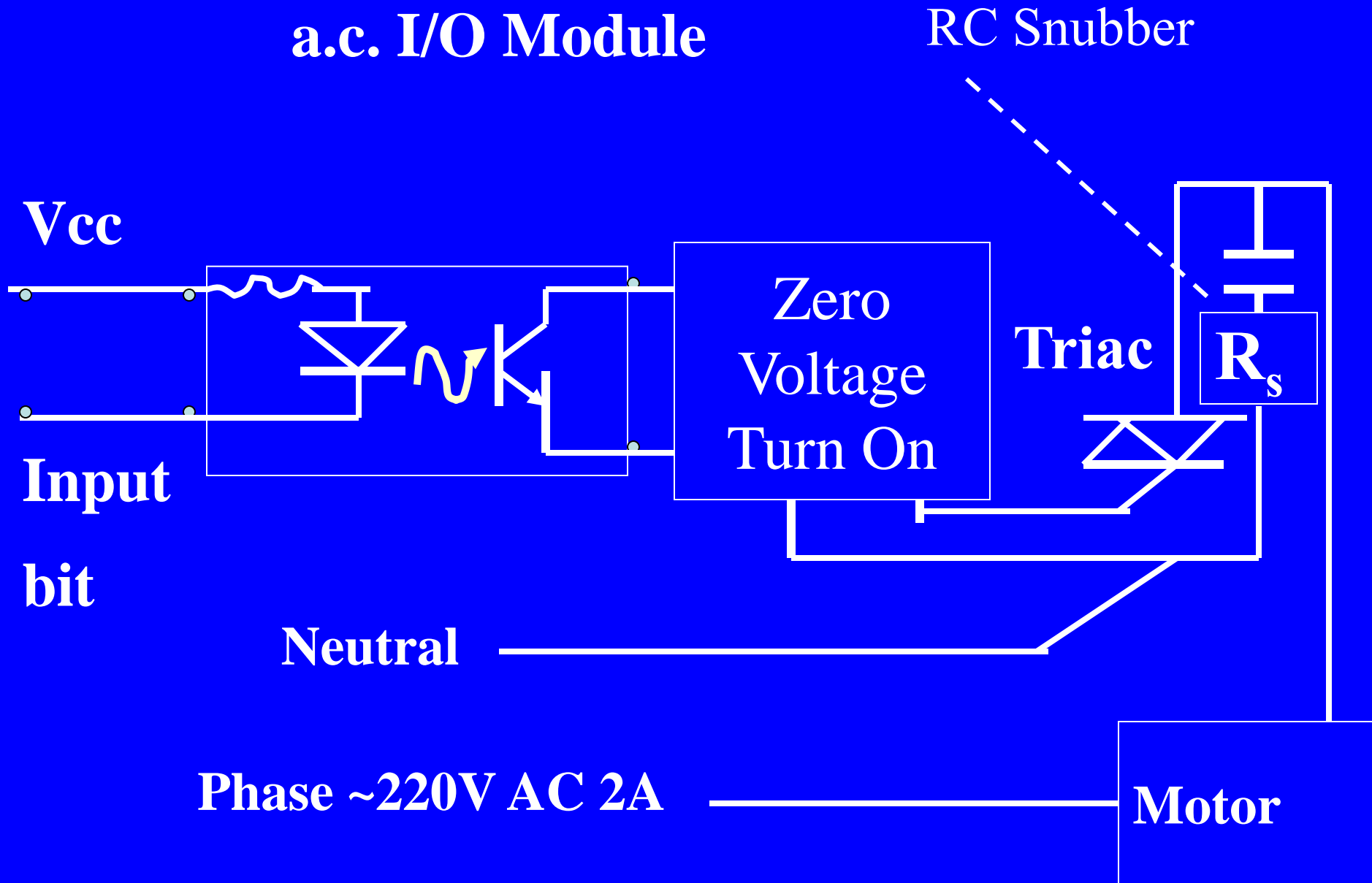

a.c. I/O Module

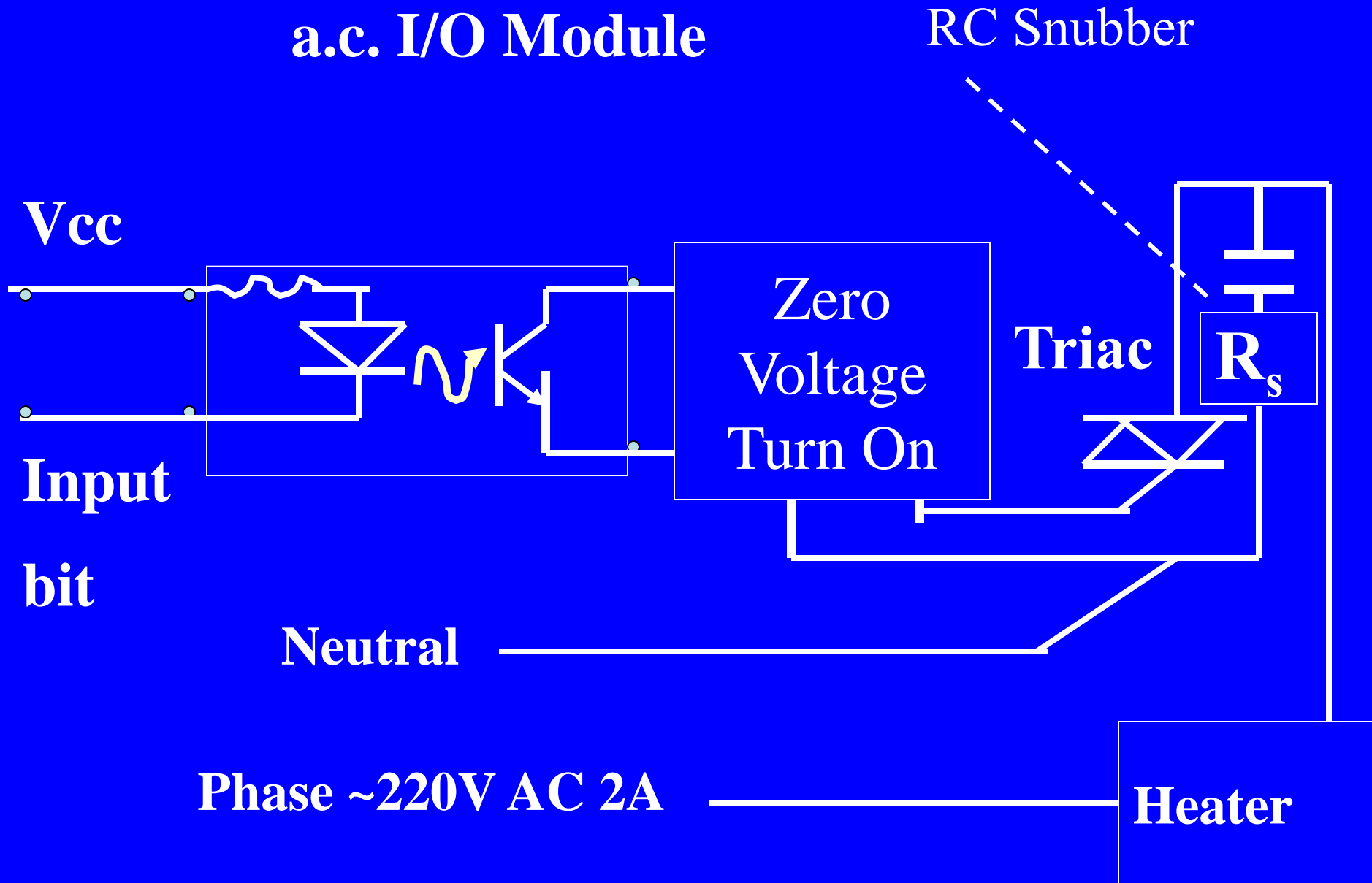

d.c. I/O Module

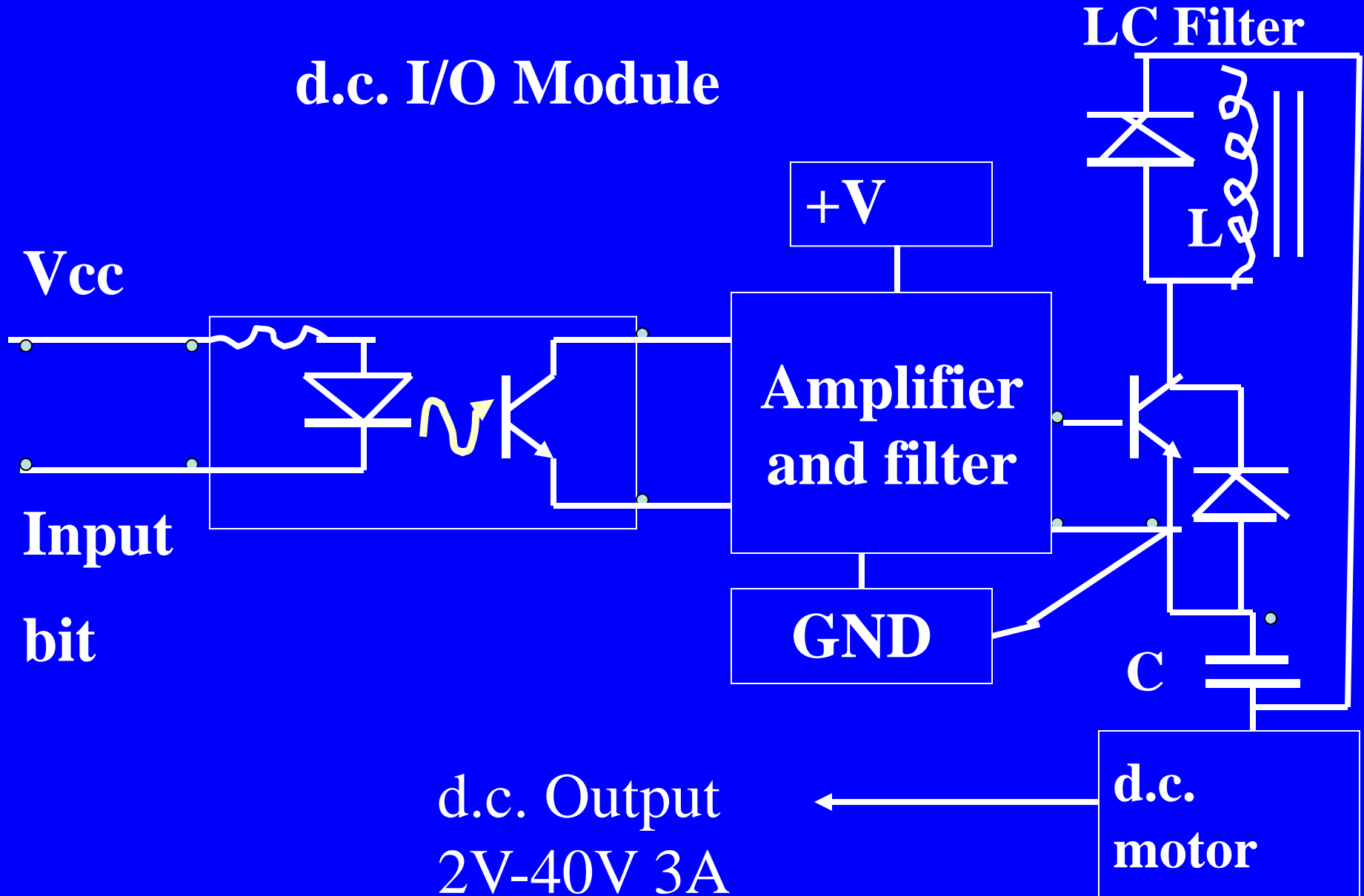

Summary

We learnt

IO Modules for High Power Devices

- Built-in Encapsulated LED-PT pair opto-isolator Protects and Isolates
- Built-in Bridge rectifier, signal conditioner, amplifier and triac circuits

We learnt

IO Modules Built-in Circuits

- Internal Reverse biased diode protector, snubber and filters
- Built-in Darlington Transistor Pair for Currents

End of Lesson 10

Interfaces for the High Power Devices